

# VHDL Design and Modeling of Combination Circuits

## Introduction

The purpose of this lab is to develop VHDL models for

## Experiment and Results

### Part 1: 0101 State Machine

```
library ieee;
use ieee.std_logic_1164.all ;
entity state_machine is
port(reset,clk,input:in bit;
                                     output: out bit);
end state_machine;

architecture state_machine of state_machine is
type Statetype is (S0,S1,S2,S3);
signal state, next_state: Statetype;
begin
state_comb: process (state,input) begin
case state is
    when S0 =>
        if input = '0' then
            next_state <= S1;
            output <= '0';

        else
            next_state <= S0;
            output <= '0';
        end if;

    when S1 =>
        if input <= '1' then
            next_state <= S2 ;
            output <='0';
        else
            next_state <=S1 ;
            output <= '0';
        end if;

    When S2 =>
        if input <='0' then
            next_state <= S3 ;
```

```

output <='0';
else
next_state <= S0;
output <= '0';
end if;

```

When S3 =>

```

if input <='1' then
next_state <= S2;
output <='1';
else
next_state <=S1;
output <= '0';
end if;

```

```

end case;
end process state_comb;


```

```

state_clocked: process
begin
wait until (clk'event and clk='1');
if reset='1' then
state <= s0;
else
state <= next_state;
end if;
end process state_clocked;
end state_machine;

```

State Machine: Simulation

 


## Part 2 Step 1: 8-Bit Adder

## 8-Bit Adder: Simulation

### Part 2 Step 2: 8-Bit Register

#### 8-Bit Register: Simulation

 

#### 8-Bit Register: VHDL Code

```
--synchronous 8-bit register
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity register8bit is
    port(
        clk:    in std_logic;
        clear:  in std_logic;
        regin:  in std_logic_vector(7 downto 0);
        regout: out std_logic_vector(7 downto 0)
    );
end register8bit;

architecture register8bit of register8bit is
begin
    process
        constant zero: std_logic_vector(7 downto 0):="00000000";
    begin
        --synchronous reset
        wait until (rising_edge(clk));

        if clear = '0' then
            regout <= zero;
        elsif clear = '1' then
            regout <= regin;
        elsif clear = 'X' or clk = 'X' then
            regout <= (others => 'X');
        end if;
    end process;
end register8bit;
```

## Part 2

### Step 1: 8-Bit Full Adder

library ieee;

use ieee.std\_logic\_1164.all;

use ieee.std\_logic\_unsigned.all;

entity adder8bit is

Port(

in1: in std\_logic\_vector (7 downto 0);

in2: in std\_logic\_vector (7 downto 0);

ci: in std\_logic;

sum: out std\_logic\_vector (7 downto 0);

co: out std\_logic);

end adder8bit;

architecture structure\_view of adder8bit is

component adder1bit

port (A,B,Cin : in std\_logic ;

Sum,Cout : out std\_logic);

end component;

signal co0, co1, co2, co3, co4, co5,co6 : std\_logic;

begin

FA0: adder1bit port map(in1(0),in2(0),ci,sum(0),co0);

FA1: adder1bit port map(in1(1),in2(1),co0,sum(1),co1);

FA2: adder1bit port map(in1(2),in2(2),co1,sum(2),co2);

FA3: adder1bit port map(in1(3),in2(3),co2,sum(3),co3);


FA4: adder1bit port map(in1(4),in2(4),co3,sum(4),co4);

FA5: adder1bit port map(in1(5),in2(5),co4,sum(5),co5);

FA6: adder1bit port map(in1(6),in2(6),co5,sum(6),co6);

FA7: adder1bit port map(in1(7),in2(7),co6,sum(7),co);

end structure\_view;

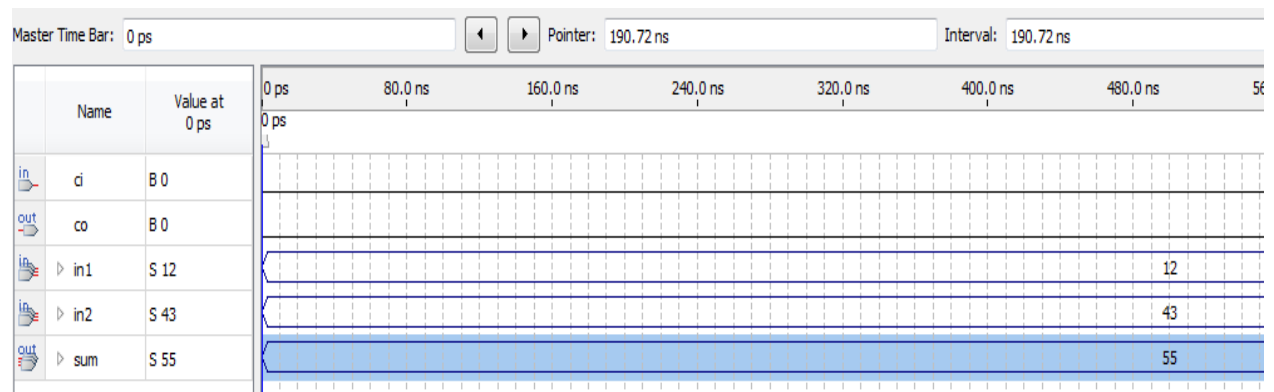

### Step 3: 8-Bit Accumulator

8-Bit Accumulator: Simulation

8-Bit Accumulator: VHDL Code